



**COLLEGE OF ENGINEERING AND MINES
DEPARTMENT OF ELECTRICAL AND COMPUTER ENGINEERING**

COURSE CODE	EE F102 F01 (CRN: 34544)		
COURSE NAME	INTRODUCTION TO ELECTRICAL AND COMPUTER ENGINEERING		
SEMESTER	SPRING		
YEAR	2022		
TYPE AND NUMBER OF SUBMISSION	HOMEWORK 3		
METHOD OF SUBMISSION	ONLINE TO : maher.albadri@alaska.edu		
DATE OF ASSIGNMENT	THURSDAY 27 JAN 2022		
DUE DATE OF SUBMISSION	FRIDAY 04 FEB 2022	DUE TIME OF SUBMISSION	23:59


STUDENT NAME	Jacob Guenther
---------------------	----------------

MAKE THIS FORM A "COVER PAGE" FOR YOUR HOMEWORK SUBMISSION.
FOR THE TA USE ONLY
REMARKS:

FOR THE TA USE ONLY		
PROBLEM NUMBER	MAXIMUM POINTS POSSIBLE	POINTS EARNED
PROBLEM 1	50	
PROBLEM 2	50	
PROBLEM 3	50	
TOTAL	150	

1 Problem HW-3-1

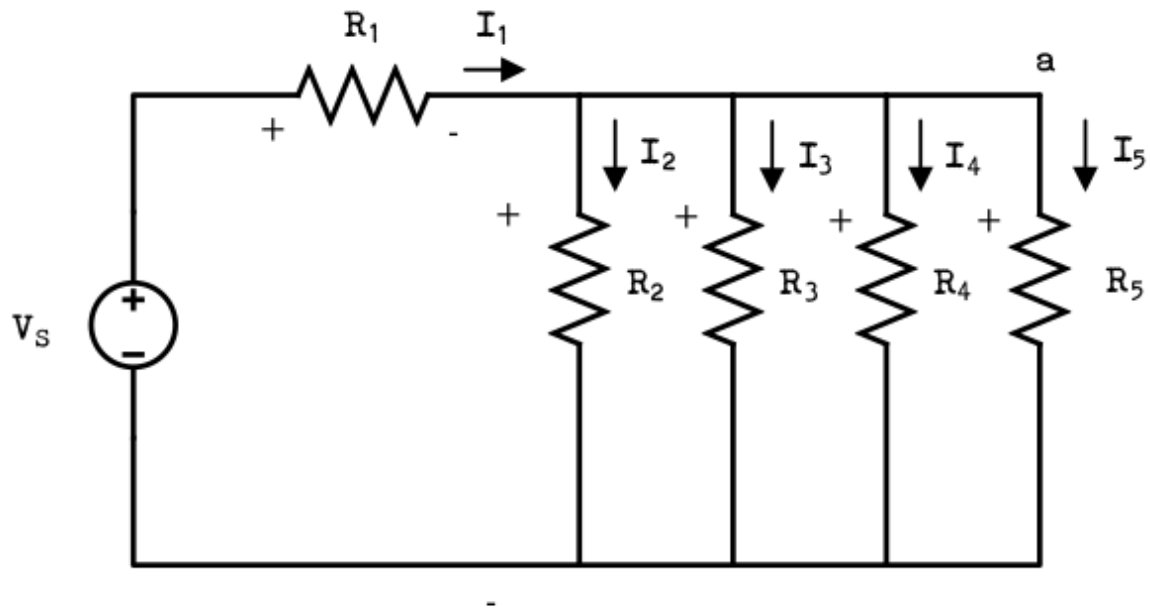- (1) For the circuit shown, measurements are conducted and the following data is made available: pts



- $V_s = 120\text{V}$
- $V_a = 73.4\text{V}$
- $P_s = 2795\text{W}$
- $P_1 = 1085\text{W}$
- $P_2 = 539\text{W}$
- $P_4 = 385\text{W}$
- $P_5 = 337\text{W}$
- (a) Determine the number of branches.
There are **6 branches** in the circuit. 5 resistors and 1 voltage source.
- (b) Determine the number of nodes.
There are **3 nodes** in the circuit.
 - between V_s and R_1
 - between R_1 , R_2 , R_3 , R_4 , and R_5
 - between R_2 , R_3 , R_4 , R_5 , and V_s
- (c) Determine the number of independent loops.

Note:

$$l = b - n + 1 \quad (1)$$

Solution:

$$\text{let } b = 6$$

$$\text{let } n = 3$$

$$l = 6 - 3 + 1$$

$$= 4 \text{ independent loops}$$

Answer: There are **4 independent loops** in the circuit.

- (d) Determine P_3 .

Note:

$$\sum P_i = 0 \quad (2)$$

Solution

$$2795\text{W} = 539\text{W} + P_3 + 385\text{W} + 337\text{W}$$

$$\begin{aligned} P_3 &= 1261\text{W} - 2795\text{W} \\ &= 1534\text{W} \end{aligned}$$

Answer: $P_3 = 1534 \text{ W}$

- (e) Determine I_1 .

Note:

$$(closedloop) \sum V_i = 0 \quad (3)$$

$$P = I \cdot V \quad (4)$$

Solution:

$$\begin{aligned} V_1 &= V_s - V_a \\ &= 120\text{V} - 73.4\text{V} \\ &= 46.6\text{V} \end{aligned}$$

$$\begin{aligned} I_1 &= \frac{1084\text{W}}{46.6\text{V}} \\ &= 23.26\text{A} \end{aligned}$$

Answer: $I_1 = 23.26 \text{ A}$

- (f) Determine I_3 .


Solution:

$$\begin{aligned} I_3 &= \frac{P_3}{V_a} \\ &= \frac{1534\text{W}}{73.4\text{V}} \\ &= 20.9\text{A} \end{aligned}$$

Answer: $I_3 = 20.9 \text{ A}$

2 Problem HW-3-2

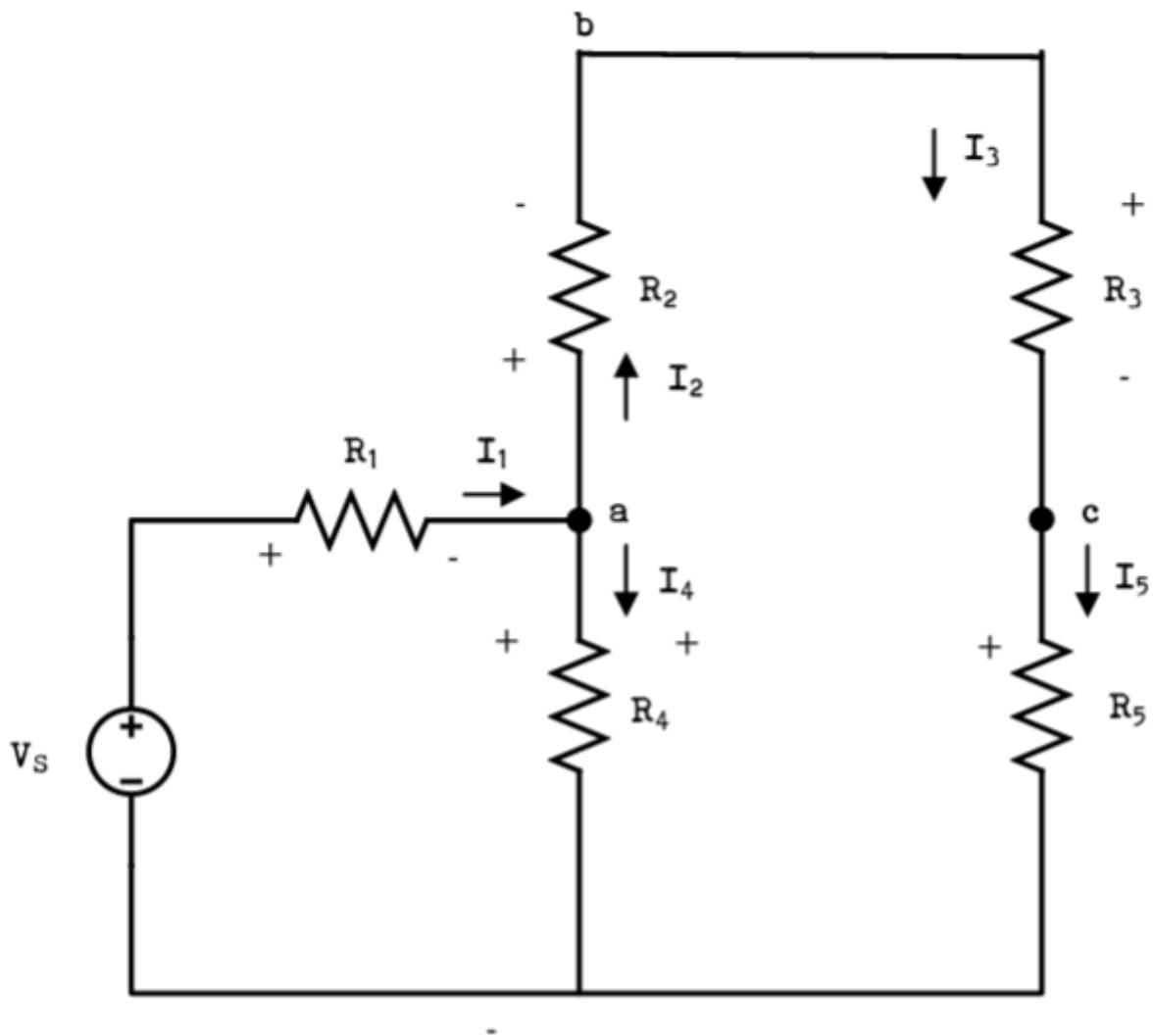- (1) For the circuit shown, measurements are conducted and the following data is made available: pts



- $V_s = 120\text{V}$
- $V_a = 72\text{V}$
- $V_b = 48\text{V}$
- $V_c = 24\text{V}$
- $P_s = 1152\text{W}$
- $P_1 = 460.8\text{W}$
- $I_4 = 7.2\text{A}$
- (a) Determine the number of branches.
There are **6 branches** in the circuit. 5 resistors and 1 voltage source.
- (b) Determine the number of nodes.
There are **5 nodes** in the circuit.
 - between V_s and R_1
 - between R_1 , R_2 , and R_4
 - between R_2 , and R_3
 - between R_3 , and R_4
 - between V_s , R_4 , and R_5

- (c) Determine the number of independent loops.

Solution:

$$\begin{aligned}\text{let } b &= 6 \\ \text{let } n &= 5 \\ l &= 6 - 5 + 1 \\ &= 2 \text{ independent loops}\end{aligned}$$

Answer: There are **2 independent loops** in the circuit.

- (d) Determine V_{ac} . **Note:**

$$\text{Note } V_a = 72\text{V}$$

$$\text{Note } V_c = 24\text{V}$$

$$\begin{aligned}V_{ac} &= V_a - V_c \\ &= 72\text{V} - 24\text{V} \\ &= 48\text{V}\end{aligned}$$

Answer: $V_{ac} = 48 \text{ V}$

- (e) Determine P_2 .

Note:

$$\sum I_{in} = \sum I_{out} \quad (5)$$

Solution:

$$\begin{aligned}V_1 &= 120\text{V} - 72\text{V} \\ &= 48\text{V}\end{aligned}$$

$$\begin{aligned}I_1 &= \frac{P_1}{V_1} \\ &= \frac{460.8\text{W}}{48\text{V}} \\ &= 9.6\text{A}\end{aligned}$$

$$I_1 = I_2 + I_4$$

$$\begin{aligned}I_2 &= 9.6\text{A} - 7.2\text{A} \\ &= 2.4\text{A}\end{aligned}$$

$$\begin{aligned}V_2 &= V_{ab} \\ &= V_a - V_b \\ &= 72\text{V} - 48\text{V} \\ &= 24\text{V}\end{aligned}$$

$$\begin{aligned}P_2 &= I_2 \cdot V_2 \\ &= 2.4\text{A} \cdot 24\text{V} \\ &= 57.6\text{W}\end{aligned}$$

Answer: $P_2 = 57.6 \text{ W}$

- (f) Determine P_3 .

Note:

$$V_b = 48\text{V}$$

$$V_c = 24\text{V}$$

$$I_2 = 2.4\text{A}$$

Solution:

$$\begin{aligned}I_2 &= I_3 \\I_3 &= 2.4\text{A} \\V_{bc} &= V_b - V_c \\&= 48\text{V} - 24\text{V} \\&= 24\text{V} \\P_3 &= I_3 \cdot V_{ab} \\&= 2.4\text{A} \cdot 24\text{V} \\&= 57.6\text{W}\end{aligned}$$

Answer: $P_3 = 57.6 \text{ W}$

- (g) Determine P_4 .

Note:

$$\begin{aligned}V_a &= 72\text{V} \\I_4 &= 7.2\text{A}\end{aligned}$$

Solution:

$$\begin{aligned}P_4 &= I_4 \cdot V_a \\&= 7.2\text{A} \cdot 72\text{V} \\&= 518.4\text{W}\end{aligned}$$

Answer: $P_4 = 518.4 \text{ W}$

- (h) Determine P_5 .

Note:

$$\begin{aligned}V_c &= 24\text{V} \\I_2 &= 2.4\text{A}\end{aligned}$$


Solution:

$$\begin{aligned}I_2 &= I_3 = I_5 = 2.4\text{A} \\P_5 &= I_5 \cdot V_c \\&= 2.4\text{A} \cdot 24\text{V} \\&= 57.6\text{W}\end{aligned}$$

Answer: $P_4 = 57.6 \text{ W}$

3 Problem HW-3-1

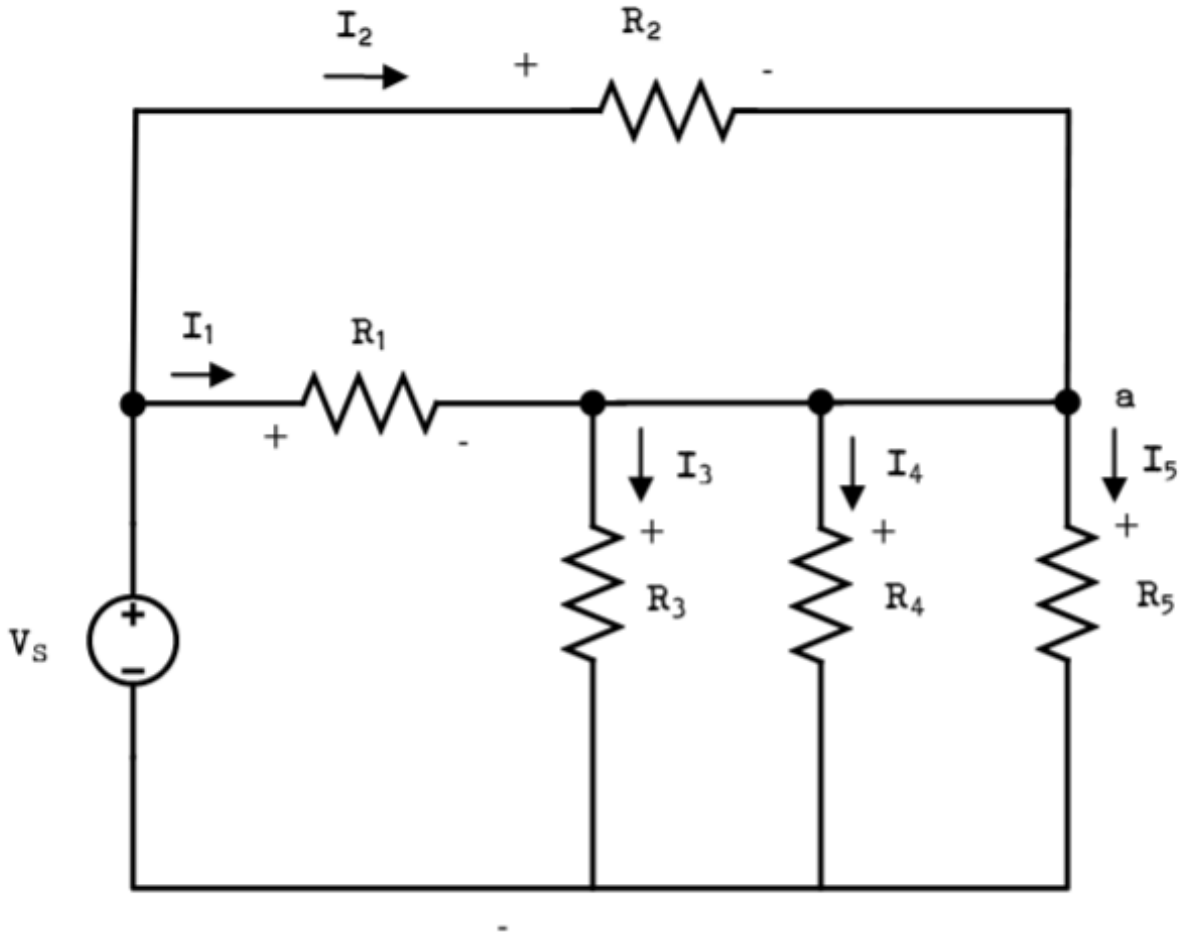- (1) For the circuit shown, measurements are conducted and the following data is made available: pts



- $V_s = 120\text{V}$
- $V_a = 48\text{V}$
- $P_s = 1728\text{W}$
- $P_1 = 518.4\text{W}$
- $P_3 = P_4 = P_5 = 230.4\text{W}$
- (a) Determine the number of branches.
There are **6 branches** in the circuit. 5 resistors and 1 voltage source.
- (b) Determine the number of nodes.
There are **3 nodes** in the circuit.
 - between V_s , R_1 , and R_2
 - between R_1 , R_2 , R_3 , R_4 , and R_5
 - between V_s , R_3 , R_4 , and R_5
- (c) Determine the number of independent loops.

let $b = 6$
 let $n = 3$
 $l = 6 - 3 + 1$
 $= 4$ independent loops

Answer: There are **4 independent loops** in the circuit.

- (d) Determine P_2 .

Solution:

$$\sum P_i = 0$$

$$0 = P_s + P_1 + P_2 + P_3 + P_4 + P_5$$

$$\begin{aligned} P_2 &= -P_s - P_1 - P_3 - P_4 - P_5 \\ &= 1728\text{W} - 518.4\text{W} - 230.4\text{W} - 230.4\text{W} - 230.4\text{W} \\ &= 518.4\text{W} \end{aligned}$$

Answer: $P_2 = 518.4 \text{ W}$

- (e) Determine I_3 .
- (f) Determine I_4 .
- (g) Determine I_5 .

Note:

$$V_a = 48\text{V}$$

$$P_3 = P_4 = P_5 = 230.4\text{W}$$

Solution:

$$\begin{aligned} I_3 &= \frac{P_3}{V_a} \\ &= \frac{230.4\text{W}}{48\text{V}} \\ &= 4.8\text{A} \end{aligned}$$

$$I_3 = I_4 = I_5 = 4.8\text{A}$$

Answer:

- (e) $I_3 = 4.8 \text{ A}$
- (f) $I_4 = 4.8 \text{ A}$
- (g) $I_5 = 4.8 \text{ A}$

4 References

- [1] Denise Thorsen, Maher Al-Badri, INTRODUCTION TO ELECTRICAL AND COMPUTER ENGINEERING, University of Alaska Fairbanks, 2022.