

# UNIVERSITY OF ALASKA FAIRBANKS COLLEGE OF ENGINEERING AND MINES DEPARTMENT OF ELECTRICAL AND COMPUTER ENGINEERING

DEPARTMENT OF ELECTRICAL AND COMPUTER ENGINEERING							
COURSE CODE		EE F102 F01 (CRN: 34544)					
COURSE NAME		INTRODUCTION TO ELECTRICAL AND COMPUTER ENGINEERING					
	_						
SEMESTER		SPRING	YE	AR	2022		
LABORATORY LOCATION		ELIF 331 (ELECTRONICS LAB)					
LAB SESSION DATE AND TIME		MONDAY 14 FEB 2022					
		•					
TYPE OF SUBMISSION		I LABORATORY REPORT		NUMBER OF SUBMISSION	4		
		•					
TITLE OF SUBMISSION		TEMPERATURE SENSOR DESIGN					
METHOD OF SUBMISSION		ONLINE TO: maher.albadri@alaska.edu					
DUE DATE OF SUBMISSION		MONDAY 21 FEB 2022		ME OF SSION	3:59		
STUDENT NAME							
MAKE THIS FORM A "COVER PAGE" FOR YOUR REPORT SUBMISSION.							
FOR THE TA USE ONLY							
REMARKS:							

# TEMPERATURE SENSOR DESIGN

# **Objective**

In this lab, you are asked to use what you have learned in the previous labs and in class to design a temperature sensor using **Thermistor** and **Arduino ATmega328p Microcontroller**.

# **Design**

Your boss has told you to design a temperature sensor capable of measuring temperature over a range of -20 °F to +70 °F. Your officemate tells you that the company has a large stock of Arduinos and thermistors you can use. Design a circuit containing your thermistor which will be connected to the A0 input of the Arduino. This circuit should be optimized to give a maximum voltage difference on A0 for the range of desired temperatures.

#### **Procedure**

1. Build up the diagram shown in **Figure 1** using your lab kit components.

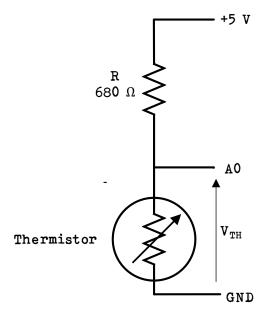


Figure 1. Circuit diagram.

The circuit should be similar to the one shown in **Figure 2**.

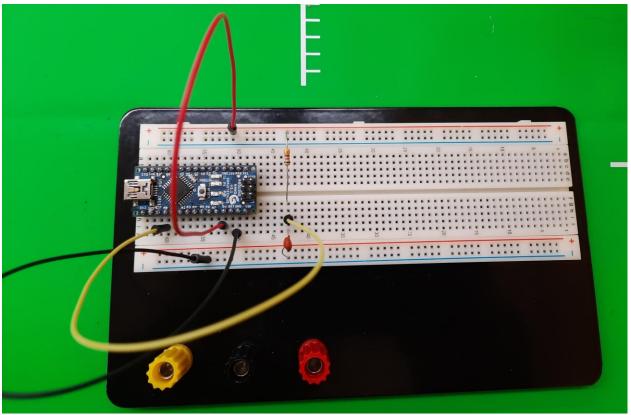


Figure 2. Built circuit.

This is a voltage divider system. We know that the thermistor changes its resistance ( $R_{TH}$ ) according to the temperature ( $T_{TH}$ ). When  $R_{TH}$  changes, it will change the voltage drop across itself, which is the voltage across A0 and the ground point GND which are information that are fed to the microcontroller. Thus, we need to make this change in voltage to be processed in the microcontroller via a proper coding, which will finally produce the temperature information. This can be carried out using the following logic.

2. Check your thermistor model and look into the datasheet provided in the appendix of this document. Look at the graph seen in the datasheet. The temperature range is -30°C to 120°C. Use the following formula to convert °C to °F:

$${}^{o}F = \frac{9}{5} {}^{o}C + 32 \tag{1}$$

Thus, the range is -22°F to 248°F. This confirms that Thermistor 103 meets the design requirements (-20°F to 70°F).

3. For **Thermistor 103**, the following data are found:

Resistance (R <sub>2</sub> )		Resistance Temp (T2) Coeff
at 25 °C (Ω)	B Constant 25/50 °C (K)	25 °C (%/°C)
10,000	4,100	-4.6

4. We use the following formula, seen in the datasheet, which relates the temperature to the thermistor resistance.

$$R_{TH} = R_2 e^{B\left(\frac{1}{T_{TH}} - \frac{1}{T_2}\right)} \tag{2}$$

The temperatures  $T_{TH}$  and  $T_2$ , in equation (2), must be in Kelvin. To convert from  ${}^{\circ}$ C to K, we use the following formula,

$$K = {}^{o}C + 273.15 \tag{3}$$

5. The outcome of the previous step is the value of  $R_{TH}$  that corresponds to the variable temperature  $T_{TH}$ . This value corresponds to the voltage across A0 and the ground point GND, let's call it  $V_{TH}$ . This relationship between  $R_{TH}$  and  $V_{TH}$  can be expressed by the voltage divider rule, as follows:

$$V_{TH} = 5 \text{ V} \frac{R_{TH}}{R_{TH} + R} \tag{4}$$

6. Equation (4) indicates that by measuring the voltage  $V_{TH}$ , the resistance  $R_{TH}$  can be determined as follows:

$$R_{TH} = \frac{V_{TH}R}{5 - V_{TH}} \tag{5}$$

7. Equation (2) will be used in equation to determine the thermistor temperature  $T_{TH}$ . Equation (2) can be rewritten as follows:

$$T_{TH} = \frac{1}{\frac{1}{B}ln\left(\frac{R_{TH}}{R_2}\right) + \frac{1}{T_2}} \tag{6}$$

8. Convert **K** to °**C** by using (7)

$${}^{o}C = K - 273.15$$
 (7)

- 9. Convert °C to °F by using (1)
- 10. All previous steps are to be coded into the microcontroller.
- 11. Thus, use the code seen in **Figure 3** as a guide to write your own code. You can create your own comments for each coding line based on your understanding.

```
temp_sensor | Arduino 1.8.19 (Windows Store 1.8.57.0)
                                                                                              \times
File Edit Sketch Tools Help
temp_sensor
 * EE F102 Spring 2022
 * Laboratory 4
 * Temperature Sensor Design
//component constants
int B = 4100;
int R2 = 10000;
float T2 = 298.15;
int R1 = 680;
float Vcc = 4.8; //measured between 5V and GND pins
void setup() {
 //setup serial connection
 Serial.begin(9600);
}
void loop() {
 // put your main code here, to run repeatedly:
 int tempVal = analogRead(A0); //sample temperature
 Serial.print("Temp sample: ");
  Serial.print(tempVal);
 float tempVolt = tempVal*Vcc/1023; //convert analog sample to voltage
  Serial.print("\tTemp voltage: ");
  Serial.print(tempVolt);
  float tempRes = tempVolt*Rl/(Vcc-tempVolt); //convert voltage to thermistor resistance
  Serial.print("\tTemp resistance: ");
  Serial.print(tempRes);
  Serial.print("\tTemp in Kelvin: ");
  Serial.print(tempKel);
  float tempCel = tempKel - 273.15;
  Serial.print("\tTemp in Celsius: ");
  Serial.print(tempCel);
  float tempFahr = tempCe1*9/5 + 32; //convert temperature in Kelvin to Fahrenheit
  Serial.print("\tTemp in Fahrenheit: ");
  Serial.print(tempFahr);
 Serial.print("\n");
 delay(2000);
}
Done Saving.
```

Figure 3. Lab 4 sketch.

- 12. **Run** the program and collect at least **10 different temperatures**. You can change the thermistor temperature by merely touching it.
- 13. **Tabulate** your data and include them into your report. **The table shall have a proper caption**.
- 14. Now, try to use your **Lab 3** skills to assign two different LEDs that respond to two different temperatures (*High* and *Low*). For example RED for high temperature, and GREEN for low temperature. To achieve this, you will need to add similar setup of Lab 3 to this lab setup. You will also need to add similar code of Lab 3 to the current code of this lab.
- 15. Once you are successful, use your smartphone to take two photographs of your setup that shows both cases (Red and Green lights). **Add the 2 photographs to your report with captions**.
- 16. **Copy** the program's modified code and paste it into your report.
- 17. Also, include a screenshot of your code into your report with a proper caption.


## Question

1. Discuss how this design was optimized based on the chosen 680  $\Omega$ . Meaning, what change would happen if we choose the 1 k $\Omega$  resistor instead of the 680  $\Omega$ .

# NTC THERMISTOR

Model No.	Resistance at $25^{\circ}C(\Omega)$	B Contant 25/50°C (K)	Resistance Temp. Coeff 25°C(%/°C)
NTC-700 NTC-900 NTC-101 NTC-121 NTC-121 NTC-121 NTC-201 NTC-201 NTC-271 NTC-271 NTC-301 NTC-401 NTC-501 NTC-681 NTC-102 NTC-152 NTC-152 NTC-152 NTC-202 NTC-252 NTC-202 NTC-502 NTC-502 NTC-503 NTC-153 NTC-153 NTC-103 NTC-103 NTC-104 NTC-104 NTC-104 NTC-104 NTC-204 NTC-204 NTC-204	70 90 100 120 150 200 220 250 270 300 400 500 680 1,000 2,500 3,000 4,000 5,000 6,800 10,000 15,000 68,000 10,000 68,000 100,000 68,000 100,000 150,000 200,000 200,000	3,100 3,100 3,100 3,100 3,100 3,100 3,100 3,100 3,100 3,100 3,100 3,500 3,800 3,800 3,800 3,900 3,900 3,900 4,100 4,100 4,100 4,200 4,200 4,400 4,400 4,400 4,500 4,500 4,600	-3.5 -3.5 -3.5 -3.5 -3.5 -3.5 -3.5 -3.5
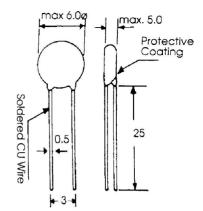
### FOR TEMPERATURE COMPENSATION 5..Ø NTC SERIES



\* Resistance Value allowable difference.

j	К	L	М
±5%	±10%	±15%	±20%

- B-Constant deviation :±10%(Calculated by R25 & R50)
  Thermal dissipation factor
  Thermal time constant
  Operating temp. range
  Max. Allowable power (25°C): 0.55W

Jameco Part Number 207036

#### PHYSICAL PROPERTIES

RESISTANCE - TEMPERATURE CHARACTERISTICS

of the termistors is the relation between of the termistors is the felation between resistance & temperature, the expression as follows:

(1) R1=R2 exp B (1/T1 - 1/T2)

WHERE: R1 is the resistance value at absolute temperature T1

R2 is the resistance value at absolute temperature T2 B is a constant depending on each thermistor

(2) According to the above formula, B can be expressed by:

B=Ln(R1/R2)/(1/T1 - 1/T2)

#### TEMPERATURE COEFFICIENT OF RESISTANCE


(\*) originates from the above formula (1), the expression as follows:  $\kappa = -B/T$ :

#### **DISSIPATION CONSTANT**

(δ) is defined for power in milliwafts necessary for rasising temperature of the thermistor by 1°C, as follows: δ =P/at (mW°C) (P: POWERΔt: rasie temperature)
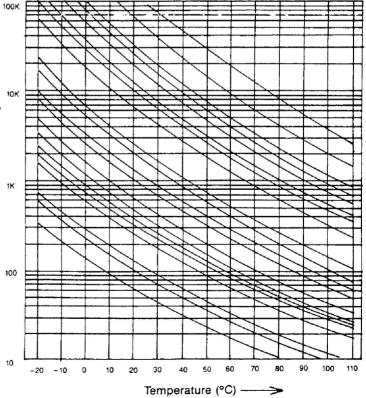
#### TIME CONSTANT (T.C.)

is regard as the time required for a thermistor to change 63% of the difference between its initial and final temperature.



NTC SENSOR Thermistors Assembly

HOW TO ORDER

NTC-

Assembly