



**COLLEGE OF ENGINEERING AND MINES
DEPARTMENT OF ELECTRICAL AND COMPUTER ENGINEERING**

COURSE CODE	EE F102 F01 (CRN: 34544)		
COURSE NAME	INTRODUCTION TO ELECTRICAL AND COMPUTER ENGINEERING		
SEMESTER	SPRING		
YEAR	2022		
TYPE AND NUMBER OF SUBMISSION	HOMEWORK 3		
METHOD OF SUBMISSION	ONLINE TO : maher.albadri@alaska.edu		
DATE OF ASSIGNMENT	THURSDAY 27 JAN 2022		
DUE DATE OF SUBMISSION	FRIDAY 04 FEB 2022	DUE TIME OF SUBMISSION	23:59

STUDENT NAME	
---------------------	--


MAKE THIS FORM A "COVER PAGE" FOR YOUR HOMEWORK SUBMISSION.
FOR THE TA USE ONLY
REMARKS:

FOR THE TA USE ONLY		
PROBLEM NUMBER	MAXIMUM POINTS POSSIBLE	POINTS EARNED
PROBLEM 1	50	
PROBLEM 2	50	
PROBLEM 3	50	
TOTAL	150	

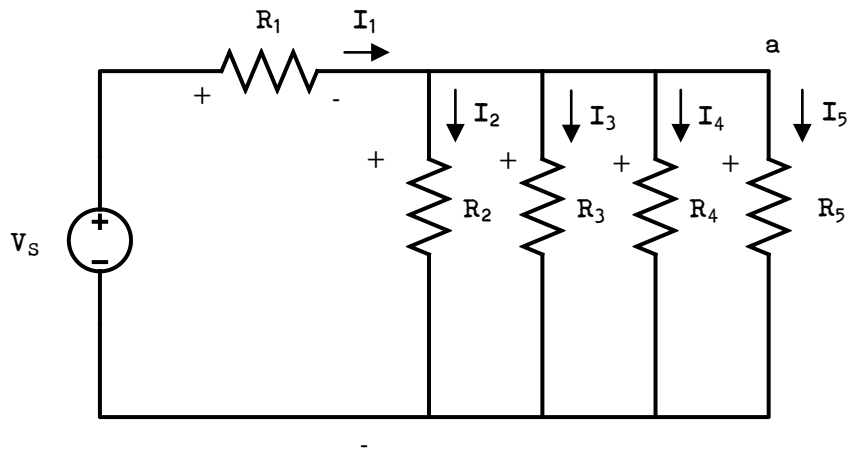Problem HW-3-1

Points
Distribution

For the circuit shown, measurements are conducted and the following data is made available:



$V_S = 120 \text{ V}$
 $V_a = 73.4 \text{ V}$
 $P_S = 2795 \text{ W}$
 $P_1 = 1085 \text{ W}$
 $P_2 = 539 \text{ W}$
 $P_4 = 385 \text{ W}$
 $P_5 = 337 \text{ W}$


- Determine the number of branches. (5)
- Determine the number of nodes. (5)
- Determine the number of independent loops. (5)
- Calculate P_3 . (10)
- Calculate I_1 . (10)
- Calculate I_3 . (15)

*** **

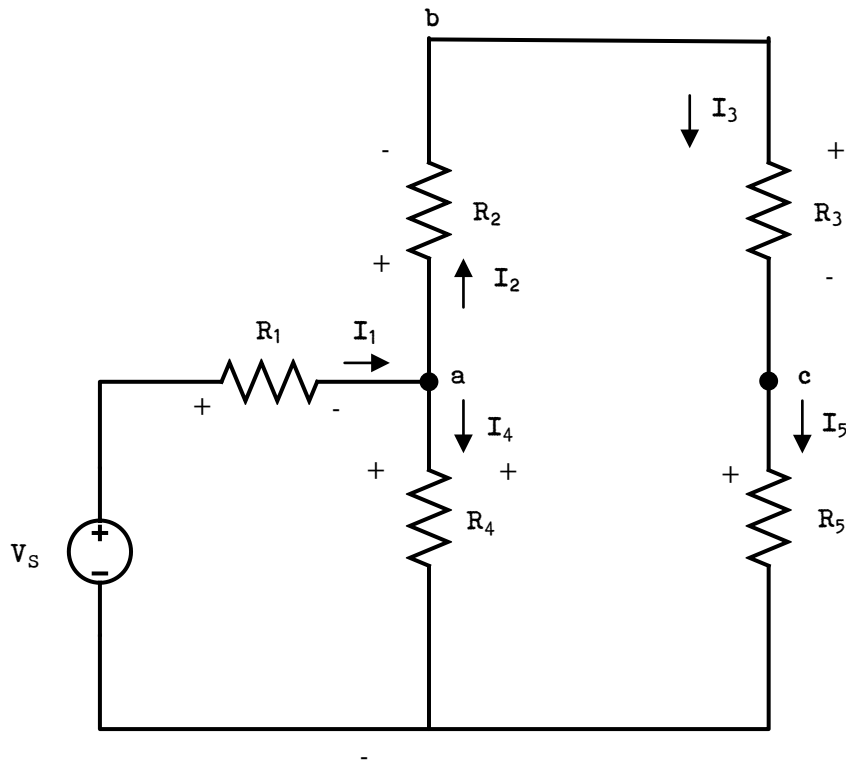Problem HW-3-2

Points
Distribution

For the circuit shown, the following data are obtained via measurements:



$V_S = 120 \text{ V}$
 $V_a = 72 \text{ V}$
 $V_b = 48 \text{ V}$
 $V_c = 24 \text{ V}$
 $P_S = 1152 \text{ W}$
 $P_1 = 460.8 \text{ W}$
 $I_4 = 7.2 \text{ A}$


- Determine the number of branches. (5)
- Determine the number of nodes. (5)
- Determine the number of independent loops. (5)
- Determine V_{ac} . (5)
- Determine P_2 . (15)
- Determine P_3 . (5)
- Determine P_4 . (5)
- Determine P_5 . (5)

*** **

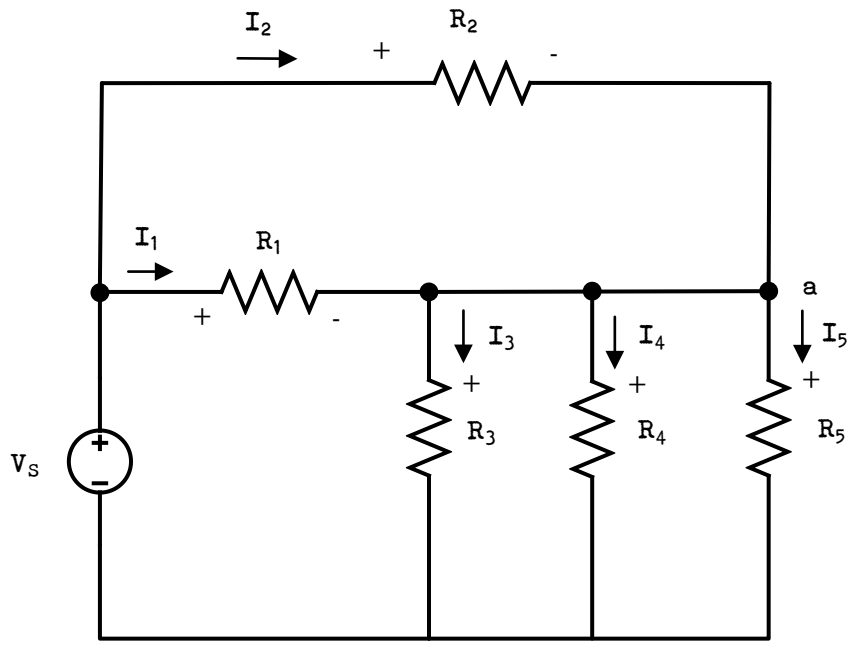Problem HW-3-3

Points
Distribution

For the circuit shown, the following quantities are measured and recorded:



$$V_S = 120 \text{ V}$$

$$V_a = 48 \text{ V}$$

$$P_S = 1728 \text{ W}$$

$$P_1 = 518.4 \text{ W}$$

$$P_3 = P_4 = P_5 = 230.4 \text{ W}$$

- Determine the number of branches. (5)
- Determine the number of nodes. (5)
- Determine the number of independent loops. (5)
- Determine P_2 . (20)
- Determine I_3 . (5)
- Determine I_4 . (5)
- Determine I_5 . (5)

*** ** *